SARDAR VALLABHBHAI NATIONAL INSTITUTE OF TECHNOLOGY

SURAT-395007, GUJARAT, INDIA



DEPARTMENT OF ELECTRONICS ENGINEERING

EC204: LINEAR INTEGRATED CIRCUITS AND APPLICATIONS (LICA)

FUNCTION GENERATOR USING IC741

PROJECT TEAM

No.	Name	Roll No.
1	Mohammed Aaftab	U23EC023
2	Arundhathi Aditya	U23EC025
3	Daksh Trivedi	U23EC026
4	Aditya Barot	U23EC027

Submission Date: April 24, 2025

Aim:

Design and Implement the circuits using IC741 and other components which generate sine wave, square wave and triangular wave.(Function Generator)

Theory :

A Function Generator is an essential instrument in electronics used to produce periodic electrical signals. It serves as a test source for electronic circuits and systems. This project explores a cost-effective approach to generating these waveforms using the IC 741 operational amplifier.

Operational Amplifier (IC 741)

The **IC 741** is a robust, commonly used op-amp known for:

- Significant open-loop gain
- Differential input configuration
- High impedance at the input and low impedance at the output

It finds extensive application in signal processing tasks such as filtering, oscillation, integration, and amplification.

Schmitt Trigger-based Relaxation Oscillator

A Schmitt Trigger-based Relaxation Oscillator uses a Schmitt Trigger in conjunction with an RC network to generate a periodic output, typically a square wave. The Schmitt Trigger's hysteresis provides noise immunity and ensures stable oscillations.
Frequency of Oscillation is determined by the RC time constant and the threshold voltages of the Schmitt Trigger. The formula for the frequency is:

$$f = \frac{1}{2RC \cdot \ln\left(\frac{1+\beta}{1-\beta}\right)}$$

where the feedback factor β is defined as:

$$\beta = \frac{R_1}{R_1 + R_2}$$

- Operation Principle:
  - The capacitor charges through the resistor, and when its voltage reaches the Schmitt Trigger's upper threshold, the output switches to high.
  - As the capacitor discharges and reaches the lower threshold, the output switches to low.
  - This cycle repeats, generating a square wave.
- Advantages:
  - Noise immunity due to hysteresis.
  - Stable oscillations.
  - Low power consumption.

Buffer Circuit Using Op-Amp

An Op-Amp Buffer (Voltage Follower) uses an operational amplifier (op-amp) with its output connected directly to the inverting input, providing unity gain (output = input). It has high input impedance and low output impedance, making it ideal for impedance matching.

- **Key Features:**
  - High Input Impedance: Does not load the signal source.
  - Low Output Impedance: Can drive low-impedance loads.
- **Applications:**
  - Impedance matching
  - Signal isolation

Integrator Circuit

An integrator circuit is an op-amp configuration that performs the mathematical operation of integration with respect to time. It converts a varying input voltage into a linearly changing output voltage (i.e., the output is the time integral of the input).

- **Circuit Description:**
  - The input resistor (R) is connected to the inverting terminal.
  - A capacitor (C) is connected between the op-amp output and the inverting input.
  - The non-inverting input is grounded.
- **Working Principle:**
  The output voltage of the integrator is given by:

$$V_{\text{out}}(t) = -\frac{1}{RC} \int V_{\text{in}}(t)\, dt$$

  This means the output decreases (or increases) over time based on the area under the input voltage curve, with a negative sign indicating a phase inversion.
- **Applications:**
  - Signal processing (e.g., wave shaping)
  - Analog computation
  - Generating ramp signals from square waves

It produces a ramp (triangular) output when the input is a constant or square wave.

Design Calculation

Square Wave Generator(U1&U2)

- **Components:**
  - R1 = $1k\,\Omega$, R2 = $10k\,\Omega$, R3 = $470\,\Omega$
  - R4, R5 =$15k\,\Omega$, C1, C2 = $0.01\,\mu$F
  - Diodes: D1, D2 = 1N4148

- **Description:**
  This is a Schmitt trigger-based square wave generator (relaxation oscillator). The RC network (R4-R5 and C1-C2) determines the charging/discharging time constant.

- **Frequency Calculation:**
  This circuit uses positive feedback. The time period is given approximately by:

$$T \approx \frac{2R_4C_1}{\ln\left(\frac{1-\beta}{1+\beta}\right)}$$

  Where:

$$\beta = \frac{R_1}{R_1 + R_2} = \frac{1\,\text{k}\Omega}{1\,\text{k}\Omega + 10\,\text{k}\Omega} \approx 0.0909$$

  Using:

  - R4 = $15k\,\Omega$
  - C1 = $0.01\,\mu$F

$$T \approx 2 \times 15\,\text{k}\Omega \times 0.01\,\mu\text{F} \times \ln\left(\frac{1 - 0.0909}{1 + 0.0909}\right) \approx 0.3 \times \ln(1.2) \approx 0.3 \times 0.182 = 54.6\,\mu\text{s}$$

$$f = \frac{1}{T} \approx \frac{1}{54.6\,\mu\text{s}} \approx 18.3\,\text{kHz}$$

Triangular Wave Generator(U3)

- **Components:**

  - R8 = $10k\,\Omega$ R9 = $47k\,\omega$
  - C3 = $0.1\,\mu$F, C4 = $1\,\mu$F

- **Description:**
  U3 acts as an integrator converting square wave to triangular wave.

- **Frequency/Amplitude:**
  Triangular wave slope depends on:

$$V_{\text{out}} = -\frac{1}{RC}\int V_{\text{in}}\,dt$$

  So,

$$\text{Slope} = \frac{V_{\text{in}}}{R_{10} \cdot C_4}$$

  Let's assume V_{in} is square wave of $\pm$5V (example):

$$\text{Slope} = \frac{5}{20\,\text{k}\Omega \cdot 1\,\mu\text{F}} = \frac{5}{0.02} = 250\,\text{V/s}$$

  Using this, and time period **T** from square wave, peak-to-peak triangular amplitude is:

$$V_{\text{pp}} = \text{Slope} \times \frac{T}{2} = 250 \times 27.3\,\mu\text{s} = 6.825\,\text{V}$$

Sine Wave Shaping (U4)

- **Components:**
  - R12 = $1M\,\Omega$,R11 = $10k\,\Omega$
  - C5 = $0.1\,\mu$F
- **Description:**
  This is a sine wave shaper circuit, most likely a precision nonlinear wave shaper using diode feedback or RC filtering.
- **Filter Cut-off (if RC low pass):**

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi \cdot 1\,\text{M}\Omega \cdot 0.1\,\mu\text{F}} \approx 1.59\,\text{Hz}$$

Simulation

1. Software Tool Used

LTSpice was used to simulate and verify the function generator circuit design. LTSpice is a powerful and widely adopted circuit simulation tool developed by Linear Technology (now part of Analog Devices). It supports the modeling and analysis of analog, digital, and mixed-signal circuits, providing various analysis types such as transient, AC, and DC sweeps.
In this project, LTSpice played a crucial role in simulating the Function Generator, which includes square wave, triangular wave, and sine wave outputs using UA741 operational amplifiers. The software allowed us to accurately model the timing, frequency response, and waveform shaping of the circuit. With its intuitive interface and precise simulation capabilities, LTSpice enabled effective verification of the design and ensured proper functionality before hardware implementation. The tool was especially helpful in observing the behavior of integrator, Schmitt trigger, and waveform shaping stages under different component configurations.

2. Circuit Diagram

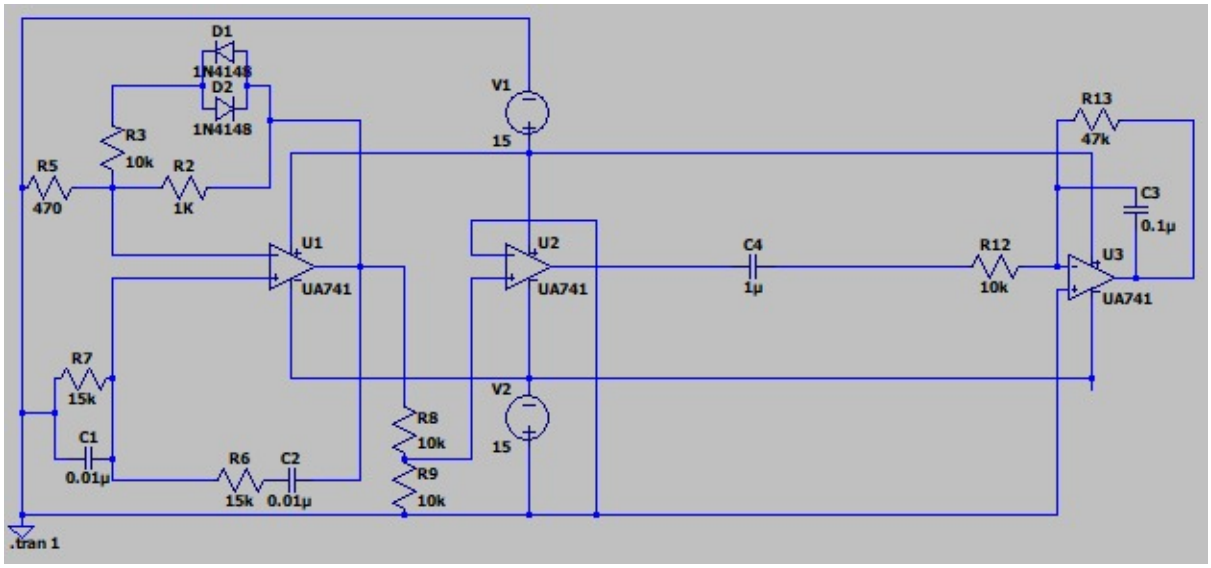


Figure 1: Output of Function Generator

3. Output

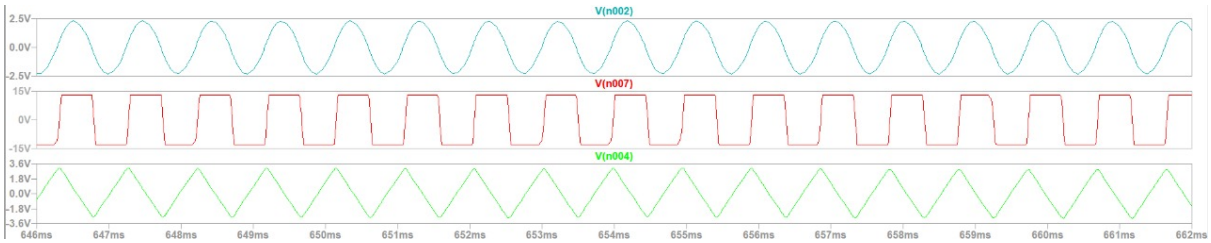


Figure 2: Circuit Diagram of Function Generator

Hardware Experiment

1. Apparatus

S. No.	Component	Rating	No. of Components Used
1	Voltage Supply	0-15 V	1
2	DSO with Probes	-	1
3	Resistors	470Ω,47kΩ,10kΩ,1MΩ,15KΩ	12
4	Capacitors	0.1 μF, 0.01 μF, 1 μF	5
5	PCB	-	1
6	IC741 (op-amp)	-	4
7	Diodes	-	2
8	Connecting Wires	-	-

2. Output of DSO

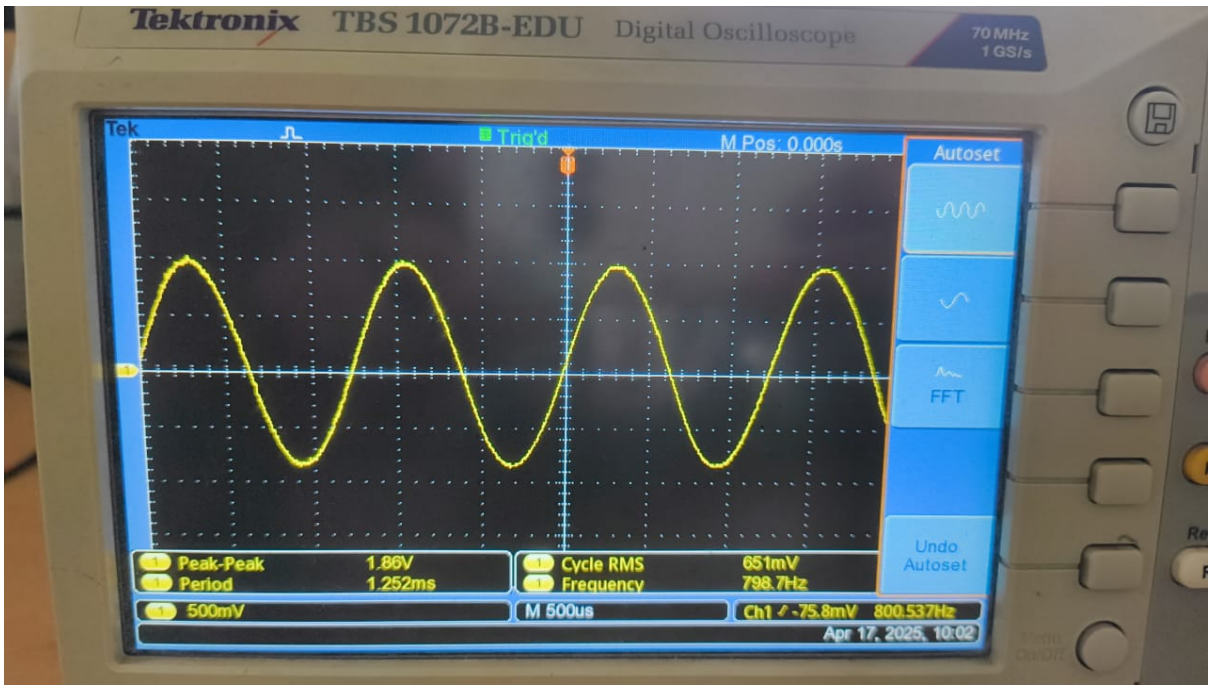


Figure 3: Sine Wave

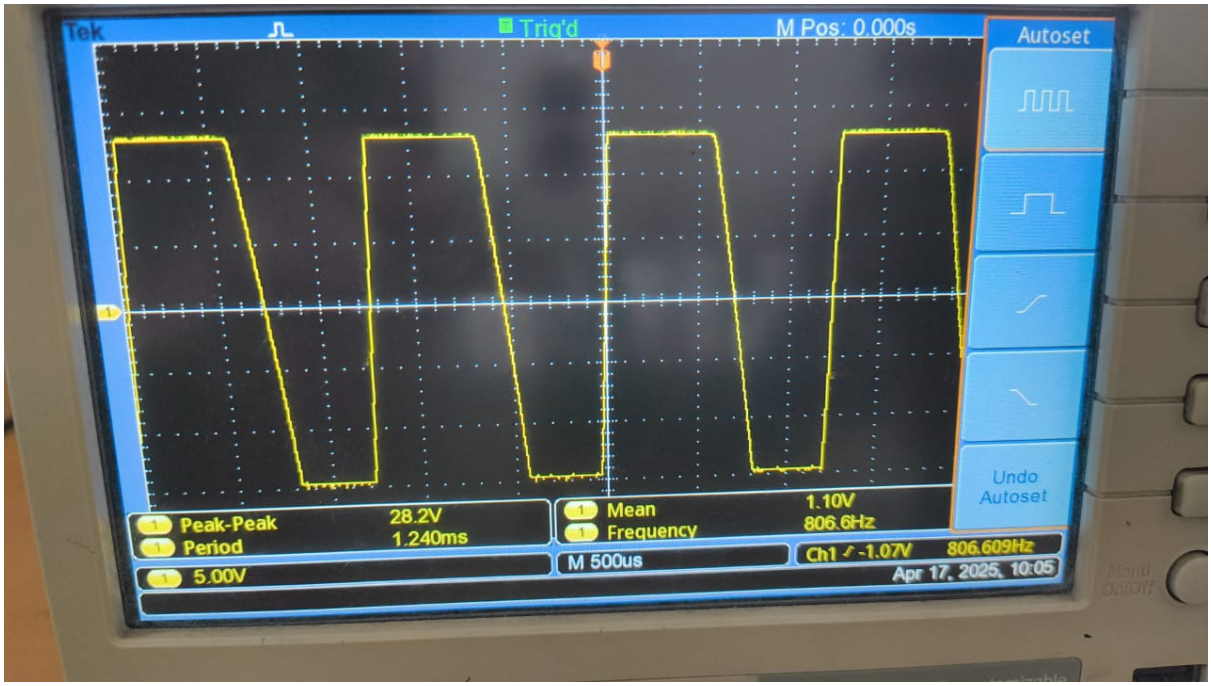


Figure 4: Square Wave

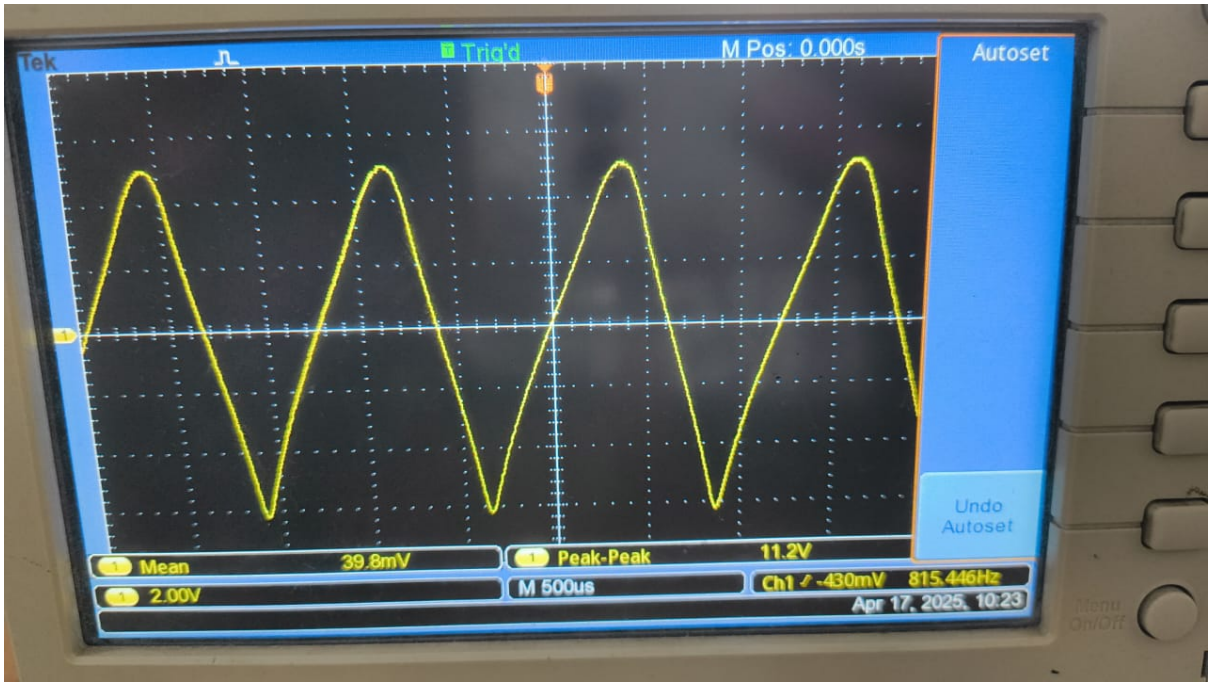


Figure 5: Triangular Wave

3. Observations

The performance of the function generator was evaluated based on the waveforms produced and their characteristics.

- Square waveform: consistent and sharp
- Triangle waveform: expected linear response
- Sine output: acceptable for low-frequency use

Conclusion

The function generator built using IC 741 successfully delivered multiple waveform outputs. With each stage contributing to waveform shaping, the circuit proved useful for analog experimentation.
Performance was dependable at lower frequencies, making it suitable for educational and prototyping environments. Minor limitations in sine shaping at higher frequencies could be mitigated with circuit refinements.

References

1. Ramakant A. Gayakwad (1999). "Op-amps and Linear Integrated Circuits"
2. Sergio Franco (2015). "Design with Operational Amplifiers and Analog Integrated Circuits"
3. IC 741 Datasheet, Texas Instruments